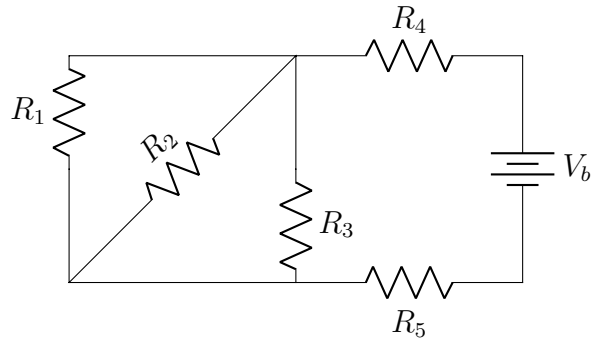


1. Consider the following circuit:



Given the following values: $V_b = 6\text{ V}$, $R_1 = 330\ \Omega$, $R_2 = 560\ \Omega$, $R_3 = 1000\ \Omega$, $R_4 = 100\ \Omega$, and $R_5 = 100\ \Omega$, determine the current through and the potential difference across each resistor.